

Digital Signal Processing

EE3900: Linear Systems and Signal Processing

Indian Institute of Technology Hyderabad

Circuits and Transforms

Shivanshu
AI21BTECH11027

7 Oct 2022

CONTENTS

- 1 **Definitions**
- 2 **Laplace Transform**
- 3 **Initial Conditions**
- 4 **Bilinear Transform**

1. DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of $g(t)$ is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

2. LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes $q_1 \mu C$. Then S is switched to position Q. After a long time, the charge on the capacitor is $q_2 \mu C$.
2. Draw the circuit using latex-tikz.

Solution: The following code yields Fig.2.2

```
wget https://github.com/Shivanshu8211/
EE3900/blob/master/Circuit/Tikz%20
Circuits/2.2.tex
```

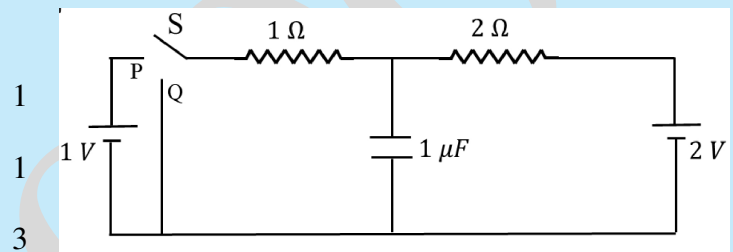


Fig. 2.1.

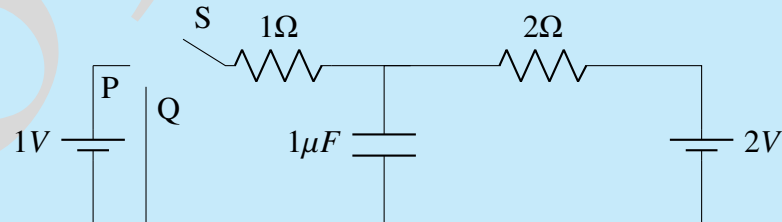


Fig. 2.2. Given Circuit

3. Find q_1 .

Solution: Before switching S to Q: Calculating

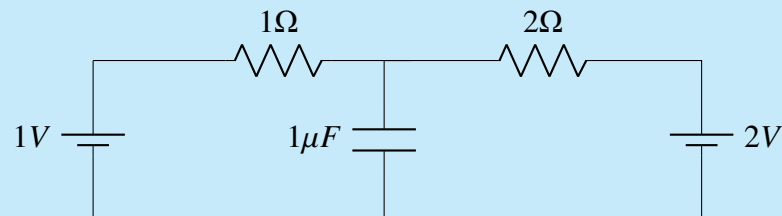


Fig. 2.3. Before switching S to Q

current,

$$1 - i - 2i - 2 = 0 \quad (2.1)$$

$$3i = -1 \Rightarrow i = \frac{-1}{3} \quad (2.2)$$

Potential Difference between capacitor at steady state is

$$1 - \left(\frac{-1}{3}\right) = \frac{4}{3} \quad (2.3)$$

$$q_1 = \frac{4}{3} \cdot 1 \quad (2.4)$$

$$= \frac{4}{3} \mu C \quad (2.5)$$

4. Show that the Laplace transform of $u(t)$ is $\frac{1}{s}$ and find the ROC.

Solution: We know that from definition of Laplace Transform,

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt U(s) = \int_0^{\infty} u(t)e^{-st} dt \quad (2.6)$$

Using (1.1),

$$U(s) = \int_0^{\infty} u(t)e^{-st} dt \quad (2.7)$$

$$= \int_0^{\infty} e^{-st} dt \quad (2.8)$$

$$= -\left(0 - \frac{1}{s}\right) \quad (2.9)$$

$$= \frac{1}{s} \quad (2.10)$$

ROC is $Re(s) > 0$ since $e^{-st} < \infty$ for $t \rightarrow \infty$. The following command plots the ROC of above Laplace Transform.

```
wget https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/codes/2.4.py
```

5. Show that

$$e^{-at}u(t) \xrightarrow{\mathcal{L}} \frac{1}{s+a}, \quad a > 0 \quad (2.11)$$

and find the ROC.

Solution: From (2.6),

$$F(s) = \int_0^{\infty} u(t)e^{-at}e^{-st} dt \quad (2.12)$$

$$= \int_0^{\infty} u(t)e^{-(s+a)t} dt \quad (2.13)$$

$$= \int_0^{\infty} e^{-(s+a)t} dt \quad (2.14)$$

$$= -\left(0 - \frac{1}{s+a}\right) \quad (2.15)$$

$$= \frac{1}{s+a} \quad (2.16)$$

ROC is

$$s+a > 0 \Rightarrow s > -a \quad (2.17)$$

The following command plots the ROC of above Laplace Transform.

```
wget https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/codes/2.5.py
```

6. Now consider the following resistive circuit transformed from Fig. 4.1 where

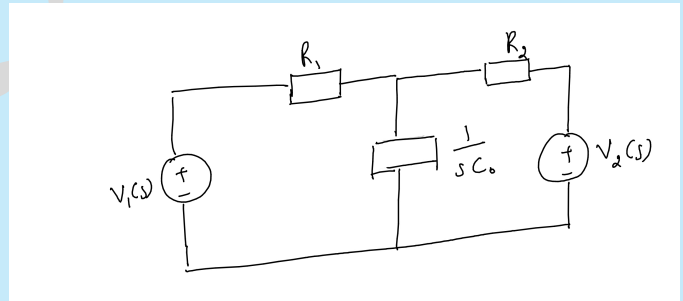


Fig. 2.4.

$$u(t) \xrightarrow{\mathcal{L}} V_1(s) \quad (2.18)$$

$$2u(t) \xrightarrow{\mathcal{L}} V_2(s) \quad (2.19)$$

Find the voltage across the capacitor $V_{C_0}(s)$.

Solution:

$$R_{eff} = \frac{1}{1 + \frac{1}{2}} = \frac{2}{3} \Omega \quad (2.20)$$

$$V_{eff} = \frac{1}{1 + \frac{1}{2}} = \frac{2}{3} V \quad (2.21)$$

$$V_{C_0}(s) = V_S(s) \frac{C_0}{C_0 + R_{eff}} \quad (2.22)$$

$$= \left(\frac{4}{3s} \right) \left(\frac{\frac{1}{s}}{\frac{1}{s} + \frac{2}{3}} \right) \quad (2.23)$$

$$= \frac{6}{s(6s + 9)} \quad (2.24)$$

7. Find $v_{C_0}(t)$. Plot using python.

Solution: Using (2.24),

$$\frac{6}{s(6s + 9)} = \frac{4}{3s} - \frac{2}{9 + 6s} \quad (2.25)$$

Apply inverse Laplacian Transform,

$$V_{C_0}(s) \xleftrightarrow{\mathcal{L}^{-1}} V_{C_0}(t) \quad (2.26)$$

$$\mathcal{L}^{-1}[V_{C_0}(s)] = \mathcal{L}^{-1} \left[\frac{4}{3s} - \frac{2}{9 + 6s} \right] \quad (2.27)$$

$$= \mathcal{L}^{-1} \left[\frac{4}{3s} \right] - \mathcal{L}^{-1} \left[\frac{2}{9 + 6s} \right] \quad (2.28)$$

Since,

$$\mathcal{L}^{-1} \left[\frac{1}{s} \right] = u(t) \quad (2.29)$$

$$\mathcal{L}^{-1} \left[\frac{1}{s - a} \right] = e^{at} u(t) \quad (2.30)$$

Using the above equations,

$$V_{C_0}(t) = \frac{4}{3} \left(1 - e^{-\frac{2}{3}t} \right) u(t) \quad (2.31)$$

The following command plots the above equation.

```
wget https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/codes/2.7.py
```

8. Verify your result using ngspice.

Solution: The following command plots the ROC of above Laplace Transform.

```
wget https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/codes/2.8.cir
python3 2.8.py
```

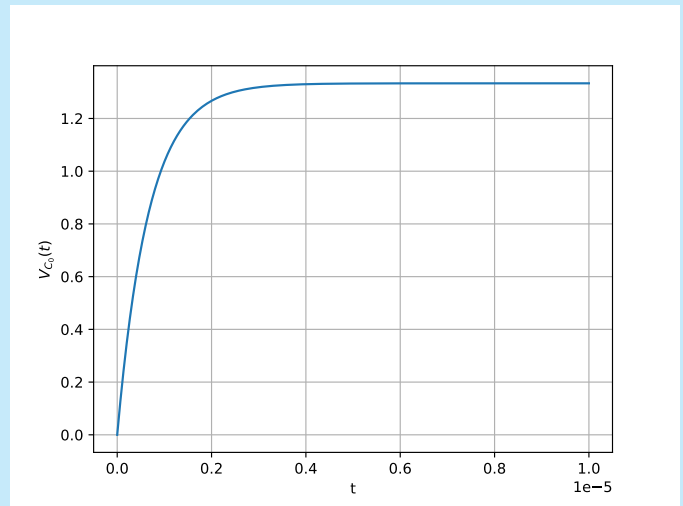


Fig. 2.5. Plot of $V_{C_0}(t)$

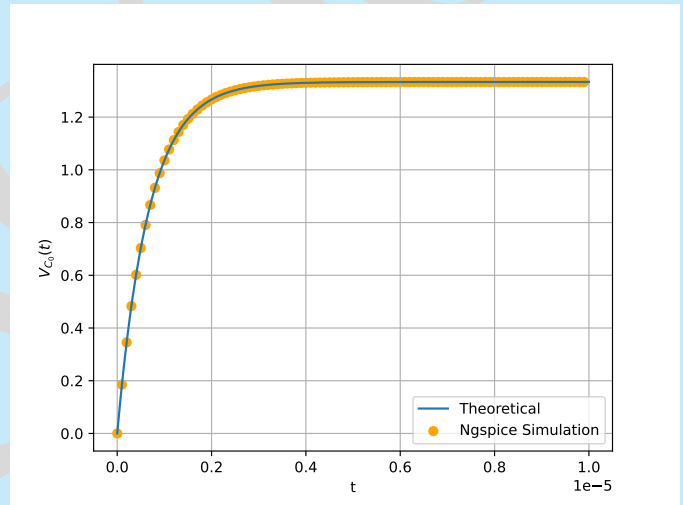


Fig. 2.6.

3. INITIAL CONDITIONS

1. Find q_2 in Fig. 4.1.

Solution: At steady state, $V_{C_0} = V_{1\Omega}$

$$V_{C_0} = \frac{q_2}{C} = V_{1\Omega} = \frac{2}{1 + 2} = \frac{2}{3}$$

$$q_2 = \frac{2}{3} \mu C$$

2. Draw the equivalent s -domain resistive circuit when S is switched to position Q. Use variables R_1, R_2, C_0 for the passive elements. Use latex-tikz.

Solution: The following command plots the ROC of above Laplace Transform.

wget <https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/Tikz%20Circuits/3.2.tex>

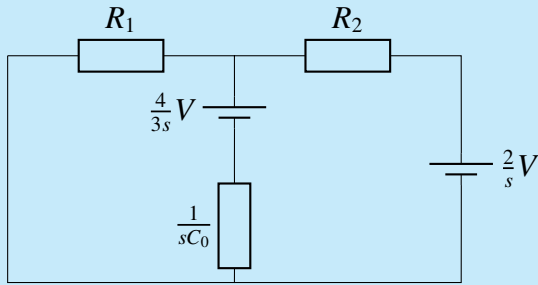


Fig. 3.1. After switching S to Q

3. $V_{C_0}(s) = ?$

Solution: Using KCL at node in Fig. 3.1

$$\frac{V-0}{R_1} + \frac{V-\frac{2}{s}}{R_2} + sC_0 \left(V - \frac{4}{3s} \right) = 0 \quad (3.1)$$

$$\Rightarrow V_{C_0}(s) = \frac{\frac{2}{sR_2} + \frac{4C_0}{3}}{\frac{1}{R_1} + \frac{2}{R_2} + sC_0} \quad (3.2)$$

4. $v_{C_0}(t) = ?$ Plot using python.

Solution: From (3.2),

$$V_{C_0}(s) = \frac{4}{3} \left(\frac{1}{\frac{1}{C_0} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) + \frac{2}{R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)} \left(\frac{1}{s} - \frac{1}{\frac{1}{C_0} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) \quad (3.3)$$

Taking an inverse Laplace Transform,

$$v_{C_0}(t) = \frac{4}{3} e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{t}{C_0}} u(t) + \frac{2}{R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)} \left(1 - e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{t}{C_0}} \right) u(t) \quad (3.4)$$

Substituting values gives

$$v_{C_0}(t) = \frac{2}{3} \left(1 + e^{-(1.5 \times 10^6)t} \right) u(t) \quad (3.5)$$

The following command plots the above equation.

wget <https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/codes/3.4.py>

5. Verify your result using ngspice.

Solution: The following command plots Fig.3.3

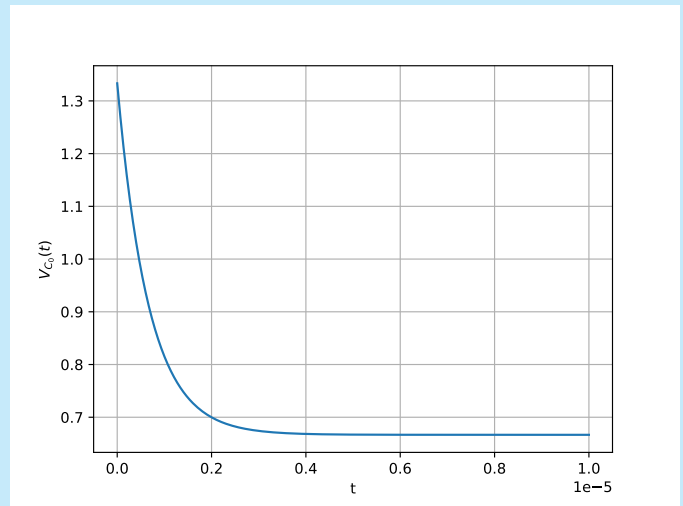


Fig. 3.2. Plot of $V_{C_0}(t)$

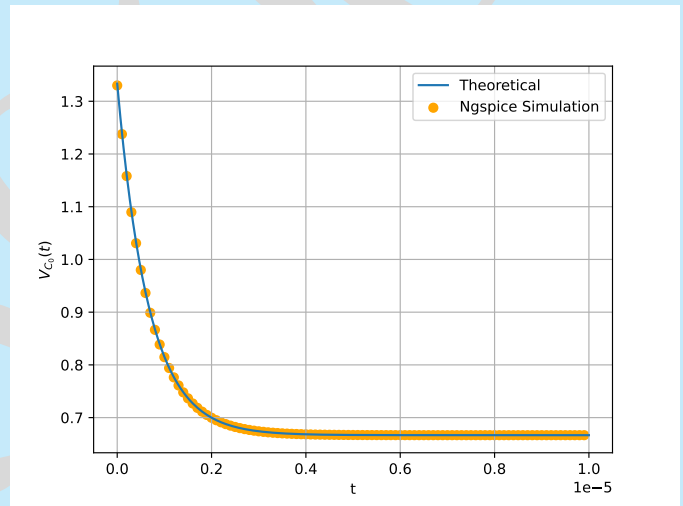


Fig. 3.3.

wget <https://github.com/Shivanshu8211/EE3900/blob/master/Circuit/codes/3.5.cir>

6. Find $v_{C_0}(0-)$, $v_{C_0}(0+)$ and $v_{C_0}(\infty)$.

Solution: From the initial conditions,

$$v_{C_0}(0-) = \frac{q_1}{C} = \frac{4}{3}V \quad (3.6)$$

Using (3.5),

$$v_{C_0}(0+) = \lim_{t \rightarrow 0+} v_{C_0}(t) = \frac{4}{3}V \quad (3.7)$$

$$v_{C_0}(\infty) = \lim_{t \rightarrow \infty} v_{C_0}(t) = \frac{2}{3}V \quad (3.8)$$

4. BILINEAR TRANSFORM

1. In Fig. 4.1, consider the case when S is

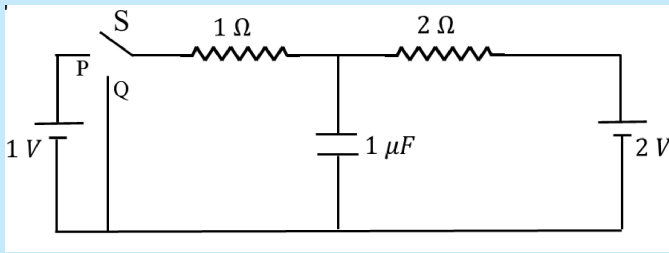


Fig. 4.1.

switched to Q right in the beginning. Formulate the differential equation. **Solution:** The required differential equation is

$$\frac{v_c(t) - 0}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + \frac{dq}{dt} = 0 \quad (4.1)$$

$$\text{i.e., } \frac{v_c(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + C_0 \frac{dv_c}{dt} = 0 \quad (4.2)$$

2. Find $H(s)$ considering the output voltage at the capacitor. **Solution:** On taking the Laplace transform on both sides of this equation

$$\frac{V_c(s)}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + sQ(s) - 0 = 0 \quad (4.3)$$

$$\Rightarrow V_c(s) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + sC_0 V_c(s) = \frac{V_2(s)}{R_2} \quad (4.4)$$

$$\Rightarrow \frac{V_c(s)}{V_2(s)} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + sC_0} \quad (4.5)$$

The transfer function is thus

$$H(s) = \frac{\frac{1}{R_2 C_0}}{s + \frac{1}{R_1 C_0} + \frac{1}{R_2 C_0}} \quad (4.6)$$

On substituting the values, we get

$$H(s) = \frac{5 \times 10^5}{s + 1.5 \times 10^6} \quad (4.7)$$


3. Plot $H(s)$. What kind of filter is it?

Solution: The given plot can be plotted using the code given below

```
wget https://github.com/Ankit-Saha-2003/EE3900/raw/main/Circuit/codes/4.3.py
```

4. Using trapezoidal rule for integration, formulate the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (4.8)$$

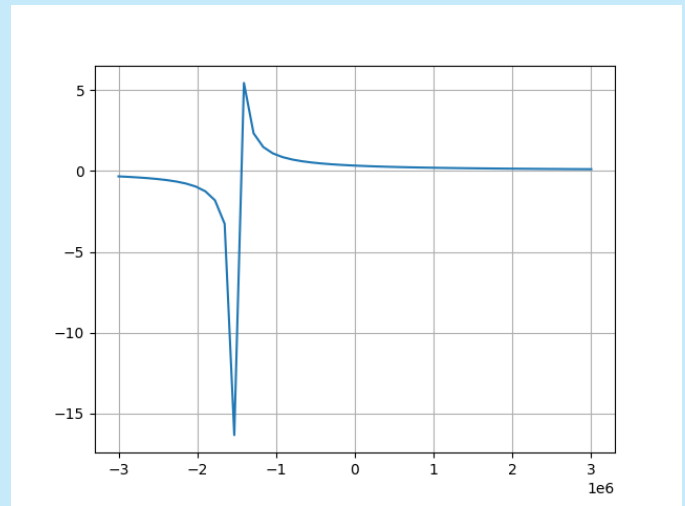Fig. 4.2. Plot of $H(s)$

Solution:

$$\frac{v_c(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + C_0 \frac{dv_c}{dt} = 0 \quad (4.9)$$

$$\Rightarrow C_0 \frac{dv_c}{dt} = \frac{2u(t) - v_c(t)}{R_2} - \frac{v_c(t)}{R_1} \quad (4.10)$$

$$\Rightarrow v_c(t)|_{t=n}^{n+1} = \int_n^{n+1} \left(\frac{2u(t) - v_c(t)}{R_2 C_0} - \frac{v_c(t)}{R_1 C_0} \right) dt \quad (4.11)$$

On doing the the above integration we will get difference equation as

$$\begin{aligned} y(n+1) & \left(1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ & = y(n) \left(1 - \frac{1}{2R_1 C_0} - \frac{1}{2R_2 C_0} \right) \\ & \quad + \frac{1}{R_2 C_0} (u(n) + u(n+1)) \end{aligned} \quad (4.12)$$

5. Find $H(z)$.

Solution: Let $\mathcal{Z}\{y(n)\} = Y(z)$

On taking the Z-transform on both sides of the difference equation

$$\begin{aligned} zY(z) & \left(1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ & = Y(z) \left(1 - \frac{1}{2R_1 C_0} - \frac{1}{2R_2 C_0} \right) \\ & \quad + \frac{1}{R_2 C_0} \left(\frac{1}{1-z^{-1}} + \frac{z}{1-z^{-1}} \right) \end{aligned} \quad (4.13)$$

$$Y(z) \left(z + \frac{z}{2R_1C_0} + \frac{z}{2R_2C_0} - 1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} \right) 7. \text{ find } y(n). \quad \text{Solution: let } a = \frac{R_1+R_2}{2C_0R_1R_2}$$

$$= \frac{1}{R_2C_0} \frac{1+z}{1-z^{-1}} \quad (4.14)$$

Also

$$v_2(t) = 2 \quad \forall t \geq 0 \quad (4.15)$$

$$\Rightarrow x(n) = 2u(n) \quad (4.16)$$

$$\Rightarrow X(z) = \frac{2}{1-z^{-1}} \quad |z| > 1 \quad (4.17)$$

Thus, the transfer function in z -domain is

$$H(z) = \frac{Y(z)}{X(z)} \quad (4.18)$$

$$= \frac{\frac{1+z}{2R_2C_0}}{z + \frac{z}{2R_1C_0} + \frac{z}{2R_2C_0} - 1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0}} \quad (4.19)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} - z^{-1} + \frac{z^{-1}}{2R_1C_0} + \frac{z^{-1}}{2R_2C_0}} \quad (4.20)$$

$$Y(z) = \frac{1+z^{-1}}{(1-z^{-1})R_2C_0(1-z^{-1} + ((1+z^{-1})(a)))} \quad (4.25)$$

$$\Rightarrow Y(z) = \frac{1+z^{-1}}{R_2C_0(1+a)(1-z^{-1})\left(1 - \frac{1-a}{1+a}z^{-1}\right)} \quad (4.26)$$

$$\Rightarrow Y(z) = \frac{1}{R_2C_0(1+a)a} \left(\frac{a+1}{1-z^{-1}} - \frac{1}{1 - \frac{(1-a)z^{-1}}{1+a}} \right) \quad (4.27)$$

$$\Rightarrow y(n) = \frac{1}{R_2C_0(1+a)a} \left((a+1)u(n) - \left(\frac{1-a}{1+a} \right)^n u(n) \right) \quad (4.28)$$

with $|z| > \min(1, \frac{|1-a|}{a+1})$. Above is for sampling period = 1s. In general, for T sampling period

$$y(nT) = \frac{T}{R_2C_0(1+aT)a} \left((aT+1)u(nT) - \left(\frac{1-aT}{1+aT} \right)^{nT} u(nT) \right) \quad (4.29)$$

s

On substituting the values

$$H(z) = \frac{2.5 \times 10^5 (1+z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.21)$$

6. How can you obtain $H(z)$ from $H(s)$?

Solution:

$$H(s) = \frac{\frac{1}{R_2C_0}}{s + \frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \quad (4.22)$$

put $s = \frac{2(1-z^{-1})}{1+z^{-1}}$ in 4.6.

$$H(z) = \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} - z^{-1} + \frac{z^{-1}}{2R_1C_0} + \frac{z^{-1}}{2R_2C_0}} \quad (4.23)$$

$$= \frac{2.5 \times 10^5 (1+z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.24)$$

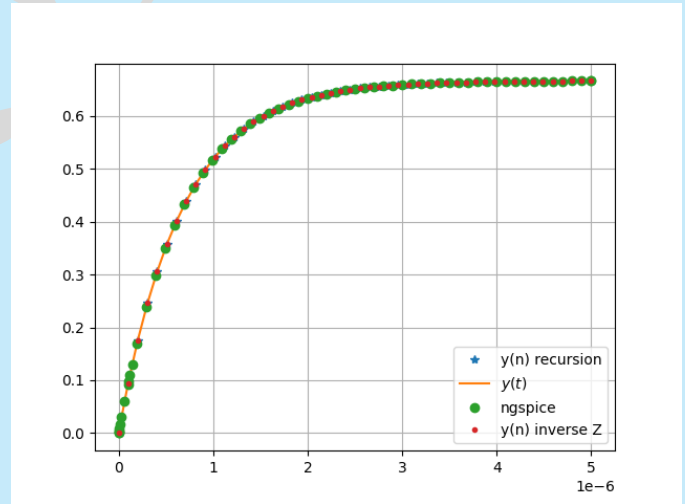


Fig. 4.3.